

Contents

Preface XV

Abbreviations XIX

1	Introduction	1
2	A Review of Network Analysis Techniques	7
2.1	Transformed Impedances	7
2.2	Nodal Analysis	9
2.3	Loop (Mesh) Analysis	9
2.4	Network Functions	11
2.5	One-Port and Two-Port Networks	12
2.5.1	One-Port Networks	12
2.5.2	Two-Port Networks	13
2.5.2.1	Admittance Matrix Parameters	13
2.5.2.2	Impedance Matrix Parameters	14
2.5.2.3	Chain Parameters (Transmission Parameters)	14
2.5.2.4	Interrelationships	15
2.5.2.5	Three-Terminal Two-Port Network	16
2.5.2.6	Equivalent Networks	16
2.5.2.7	Some Commonly Used Nonreciprocal Two-Ports	16
2.6	Indefinite Admittance Matrix	18
2.6.1	Network Functions of a Multiterminal Network	20
2.7	Analysis of Constrained Networks	24
2.8	Active Building Blocks for Implementing Analog Filters	28
2.8.1	Operational Amplifier	28
2.8.2	Operational Transconductance Amplifier	30
2.8.3	Current Conveyor	31
	Practice Problems	33
3	Network Theorems and Approximation of Filter Functions	41
3.1	Impedance Scaling	41
3.2	Impedance Transformation	42
3.3	Dual and Inverse Networks	44

3.3.1	Dual and Inverse One-Port Networks	44
3.3.2	Dual Two-Port Networks	45
3.4	Reversed Networks	47
3.5	Transposed Network	48
3.6	Applications to Terminated Networks	50
3.7	Frequency Scaling	52
3.8	Types of Filters	52
3.9	Magnitude Approximation	54
3.9.1	Maximally Flat Magnitude (MFM) Approximation	55
3.9.1.1	MFM Filter Transfer Function	56
3.9.2	Chebyshev (CHEB) Magnitude Approximation	60
3.9.2.1	CHEB Filter Transfer Function	63
3.9.3	Elliptic (ELLIP) Magnitude Approximation	65
3.9.4	Inverse-Chebyshev (ICHEB) Magnitude Approximation	68
3.10	Frequency Transformations	69
3.10.1	LP to HP Transformation	69
3.10.2	LP to BP Transformation	71
3.10.3	LP to BR Transformation	73
3.11	Phase Approximation	73
3.11.1	Phase Characteristics of a Transfer Function	74
3.11.2	The Case of Ideal Transmission	74
3.11.3	Constant Delay (Linear Phase) Approximation	75
3.11.4	Graphical Method to Determine the BT Filter Function	76
3.12	Delay Equalizers	77
	Practice Problems	78
4	Basics of Passive Filter Design	83
4.1	Singly Terminated Networks	83
4.2	Some Properties of Reactance Functions	85
4.3	Singly Terminated Ladder Filters	88
4.4	Doubly Terminated LC Ladder Realization	92
	Practice Problems	100
5	Second-Order Active-RC Filters	103
5.1	Some Basic Building Blocks using an OA	104
5.2	Standard Biquadratic Filters or Biquads	104
5.3	Realization of Single-Amplifier Biquadratic Filters	109
5.4	Positive Gain SAB Filters (Sallen and Key Structures)	111
5.4.1	Low-Pass SAB Filter	111
5.4.2	RC:CR Transformation	113
5.4.3	High-Pass Filter	115
5.4.4	Band-Pass Filter	115
5.5	Infinite-Gain Multiple Feedback SAB Filters	115
5.6	Infinite-Gain Multiple Voltage Amplifier Biquad Filters	117
5.6.1	KHN State-Variable Filter	119

5.6.2	Tow–Thomas Biquad	121
5.6.3	Fleischer–Tow Universal Biquad Structure	123
5.7	Sensitivity	124
5.7.1	Basic Definition and Related Expressions	124
5.7.2	Comparative Results for ω_p and Q_p Sensitivities	126
5.7.3	A Low-Sensitivity Multi-OA Biquad with Small Spread in Element Values	126
5.7.4	Sensitivity Analysis Using Network Simulation Tools	129
5.8	Effect of Frequency-Dependent Gain of the OA on the Filter Performance	130
5.8.1	Cases of Inverting, Noninverting, and Integrating Amplifiers Using an OA with Frequency-Dependent Gain	130
5.8.1.1	Inverting Amplifier	130
5.8.1.2	Noninverting Amplifier	131
5.8.1.3	Inverting Integrating Amplifier	132
5.8.2	Case of Tow–Thomas Biquad Realized with OA Having Frequency-Dependent Gain	132
5.9	Second-Order Filter Realization Using Operational Transconductance Amplifier (OTA)	135
5.9.1	Realization of a Filter Using OTAs	138
5.9.2	An OTA-C Band-Pass Filter	138
5.9.3	A General Biquadratic Filter Structure	139
5.10	Technological Implementation Considerations	140
5.10.1	Resistances in IC Technology	141
5.10.1.1	Diffused Resistor	141
5.10.1.2	Pinched Resistor	142
5.10.1.3	Epitaxial and Ion-Implanted Resistors	142
5.10.1.4	Active Resistors	143
5.10.2	Capacitors in IC Technology	144
5.10.2.1	Junction Capacitors	145
5.10.2.2	MOS Capacitors	145
5.10.2.3	Polysilicon Capacitor	146
5.10.3	Inductors	146
5.10.4	Active Building Blocks	147
5.10.4.1	Operational Amplifier (OA)	147
5.10.4.2	Operational Transconductance Amplifier (OTA)	148
5.10.4.3	Transconductance Amplifiers (TCAs)	150
5.10.4.4	Current Conveyor (CC)	151
	Practice Problems	152
6	Switched-Capacitor Filters	161
6.1	Switched C and R Equivalence	162
6.2	Discrete-Time and Frequency Domain Characterization	163
6.2.1	SC Integrators: $s \leftrightarrow z$ Transformations	164

6.2.2	Frequency Domain Characteristics of Sampled-Data Transfer Function	167
6.3	Bilinear $s \leftrightarrow z$ Transformation	169
6.4	Parasitic-Insensitive Structures	173
6.4.1	Parasitic-Insensitive-SC Integrators	176
6.4.1.1	Lossless Integrators	176
6.4.1.2	Lossy Integrators	177
6.5	Analysis of SC Networks Using PI-SC Integrators	177
6.5.1	Lossless and Lossy Integrators	177
6.5.1.1	Inverting Lossless Integrator	177
6.5.1.2	Noninverting Lossless Integrator	179
6.5.1.3	Inverting and Noninverting Lossless Integration Combined	179
6.5.1.4	Lossy PI-SC Integrator	181
6.5.2	Application of the Analysis Technique to a PI-SC Integrator-Based Second-Order Filter	181
6.5.3	Signals Switched to the Input of the OA during Both Phases of the Clock Signal	183
6.6	Analysis of SC Networks Using Network Simulation Tools	184
6.6.1	Use of VCVS and Transmission Line for Simulating an SC Filter	184
6.7	Design of SC Biquadratic Filters	187
6.7.1	Fleischer–Laker Biquad	188
6.7.2	Dynamic Range Equalization Technique	191
6.8	Modular Approach toward Implementation of Second-Order Filters	191
6.9	SC Filter Realization Using Unity-Gain Amplifiers	199
6.9.1	Delay-and-add Blocks Using UGA	200
6.9.2	Delay Network Using UGA	201
6.9.3	Second-Order Transfer Function Using DA1, DA2 and D Networks	202
6.9.4	UGA-Based Filter with Reduced Number of Capacitances	202
	Practice Problems	204
7	Higher-Order Active Filters	207
7.1	Component Simulation Technique	207
7.1.1	Inductance Simulation Using Positive Impedance Inverters or Gyrators	208
7.1.2	Inductance Simulation Using a Generalized Immittance Converter	210
7.1.2.1	Sensitivity Considerations	213
7.1.3	FDNR or Super-Capacitor in Higher-Order Filter Realization	213
7.1.3.1	Sensitivity Considerations	216
7.2	Operational Simulation Technique for High-Order Active RC Filters	217
7.2.1	Operational Simulation of All-Pole Filters	217
7.2.2	Leapfrog Low-Pass Filters	219

7.2.3	Systematic Steps for Designing Low-Pass Leapfrog Filters	220
7.2.4	Leapfrog Band-Pass Filters	222
7.2.5	Operational Simulation of a General Ladder Structure	223
7.3	Cascade Technique for High-Order Active Filter Implementation	225
7.3.1	Sensitivity Considerations	227
7.3.2	Sequencing of the Biquads	228
7.3.3	Dynamic Range Considerations	228
7.4	Multiloop Feedback (and Feed-Forward) System	229
7.4.1	Follow the Leader Feedback Structure	229
7.4.1.1	$T_i = (1/s)$, a Lossless Integrator	230
7.4.1.2	$T_i = 1/(s + \infty)$, a Lossy Integrator	231
7.4.2	FLF Structure with Feed-Forward Paths	233
7.4.3	Shifted Companion Feedback Structure	234
7.4.4	Primary Resonator Block Structure	237
7.5	High-Order Filters Using Operational Transconductance Amplifiers	239
7.5.1	Cascade of OTA-Based Filters	239
7.5.2	Inductance Simulation	239
7.5.3	Operational Simulation Technique	239
7.5.4	Leapfrog Structure for a General Ladder	242
7.6	High-Order Filters Using Switched-Capacitor (SC) Networks	245
7.6.1	Parasitic-Insensitive Toggle-Switched-Capacitor (TSC) Integrator	245
7.6.2	A Stray-Insensitive Bilinear SC Integrator Using Biphase Clock Signals	247
7.6.3	A Stray-Insensitive Bilinear Integrator with Sample-and-Hold Input Signal	247
7.6.4	Cascade of SC Filter Sections for High-Order Filter Realization	248
7.6.5	Ladder Filter Realization Using the SC Technique	250
	Practice Problems	251
8	Current-Mode Filters	255
8.1	Basic Operations in Current-Mode	255
8.1.1	Multiplication of a Current Signal	255
8.1.1.1	Use of a Current Mirror	256
8.1.1.2	Use of a Current Conveyor	257
8.1.1.3	Use of Current Operational Amplifier	258
8.1.2	Current Addition (or Subtraction)	259
8.1.3	Integration and Differentiation of a Current Signal	259
8.2	Current Conveyors in Current-Mode Signal Processing	264
8.2.1	Some Basic Building Blocks Using CCII	264
8.2.2	Realization of Second-Order Current-Mode Filters	264
8.2.2.1	Universal Filter Implementation	264
8.2.2.2	All-Pass/Notch and Band-Pass Filters Using a Single CCII	265
8.2.2.3	Universal Biquadratic Filter Using Dual-Output CCII	266
8.3	Current-Mode Filters Derived from Voltage-Mode Structures	267

8.4	Transformation of a VM Circuit to a CM Circuit Using the Generalized Dual	269
8.5	Transformation of VM Circuits to CM Circuits Using Transposition	271
8.5.1	CM Circuits from VM Circuits Employing Single-Ended OAs	272
8.5.1.1	CM Biquads Derived from VM Biquads Employing Finite Gain Amplifiers	272
8.5.1.2	CM Biquads Derived from VM Biquads Employing Infinite-Gain Amplifiers	273
8.5.2	CM Circuits from VM Circuits Employing OTAs	274
8.5.2.1	VM Circuits Using Single-Ended OTAs	274
8.5.2.2	VM Circuits Using Differential-Input OTAs	277
8.6	Derivation of CTF Structures Employing Infinite-Gain Single-Ended OAs	279
8.6.1	Illustrative Examples	280
8.6.1.1	Single-Amplifier Second-Order Filter Network	280
8.6.1.2	Tow-Thomas Biquad	281
8.6.1.3	Ackerberg and Mossberg LP and BP Filters	282
8.6.2	Effect of Finite Gain and Bandwidth of the OA on the Pole Frequency, and Pole Q	283
8.7	Switched-Current Techniques	285
8.7.1	Add, Subtract, and Multiply Operations	286
8.7.2	Switched-Current Memory Cell	286
8.7.3	Switched-Current Delay Cell	288
8.7.4	Switched-Current Integrators	288
8.7.5	Universal Switched-Current Integrator	290
8.8	Switched-Current Filters	291
	Practice Problems	294
9	Implementation of Analog Integrated Circuit Filters	299
9.1	Active Devices for Analog IC Filters	300
9.2	Passive Devices for IC Filters	300
9.2.1	Resistance	300
9.2.2	Switch	302
9.3	Preferred Architecture for IC Filters	303
9.3.1	OA-Based Filters with Differential Structure	303
9.3.1.1	First-Order Filter Transfer Functions	304
9.3.1.2	Second-Order Filter Transfer Functions	304
9.3.2	OTA-Based Filters with Differential Structures	310
9.3.2.1	First-Order Filter Transfer Functions	310
9.3.2.2	Second-Order Filter Transfer Functions	312
9.4	Examples of Integrated Circuit Filters	314
9.4.1	A Low-Voltage, Very Wideband OTA-C Filter in CMOS Technology	314
9.4.2	A Current-Mode Filter for Mobile Communication Application	318

9.4.2.1	Filter Synthesis	318
9.4.2.2	Basic Building Block	319
9.4.2.3	Inductance and Negative Resistance	321
9.4.2.4	Second-Order Elementary Band-Pass Filter Cell	321
	Practice Problems	323

Appendices 325**Appendix A** 327

A.1	Denominator Polynomial $D(s)$ for the Butterworth Filter Function of Order n , with Passband from 0 to 1 rad s^{-1}	327
A.2	Denominator Polynomial $D(s)$ for the Chebyshev Filter Function of Order n , with Passband from 0 to 1 rad s^{-1}	328
A.3	Denominator Polynomial $D(s)$ for the Bessel Thomson Filter Function of Order n	328
A.4	Transfer Functions for Several Second-, Third-, and Fourth-Order Elliptic Filters	330

Appendix B 333

B.1	Bessel Thomson Filter Magnitude Error Calculations (MATLAB Program)	333
B.2	Bessel Thomson Filter Delay Error Calculations (MATLAB Program)	334

Appendix C 337

C.1	Element Values for All-Pole Single-Resistance-Terminated Low-Pass Lossless Ladder Filters	337
C.2	Element Values for All-Pole Double-Resistance-Terminated Low-Pass Lossless Ladder Filters	337
C.3	Element Values for Elliptic Double-Resistance-Terminated Low-Pass Lossless Ladder Filters	340

References 345**Index** 351

