Index

a

AC current control
  control loop gains 549
  decoupling gains 559
active damping 525, 559, 659
admittance matrix 54, 636, 637, 645, 653, 655
amplitude invariance 68
average-current-mode control
  current-loop amplifier 225
  duty-ratio generation 224–226
averaged state space 7, 60, 63, 71, 73, 129, 143, 146, 149, 153, 164, 165, 167, 170, 233, 234, 279, 287, 362, 363, 367, 372, 380
average modeling 57, 60, 142

b

Bode plot 86–88, 90, 91, 312, 316, 322, 326, 327, 471–473, 477, 479
boost converter 6, 134, 136, 146, 148, 149, 167, 199, 201, 206, 211, 213, 215, 222, 238, 258, 321, 325, 345, 346, 365, 366, 397, 439, 447, 479
  power-stage 351, 352, 383, 387, 390, 397, 398, 410, 439, 440, 446, 447, 451, 457
boundary conduction mode (BCM) 58, 157
buck–boost converter 136, 138, 139, 149, 151, 170, 199, 202, 206, 207, 213, 215, 222, 227, 239, 249, 347, 368, 369, 372, 387, 469
  power-stage 352, 387
buck converter 3, 6, 7, 14, 15, 19, 61, 64, 97, 126, 127, 131–133, 135, 137, 140, 142–144, 164, 176–181, 191, 197–202, 205, 209–211, 213, 215, 222, 225, 230, 239–242, 244–248, 251, 253, 254, 269, 272, 274, 279, 280, 282, 287–289, 291–293, 298, 301, 307, 308, 312, 315, 330, 345, 346, 348, 358, 365, 414, 417, 476
  power-stage 351, 377, 380, 386, 387, 390, 397–399, 405, 406, 410, 411, 413

c

CLCL filter 112, 115
complementary sensitivity function 27, 84, 92
continuous conduction mode (CCM) 57
control bandwidth
  crossover frequency 92
  RHP pole limitation 102
  RHP zero limitation 86, 163
control block diagram
  generalized MIMO cascaded control 365
  generalized MIMO closed loop 48, 452
  generalized MIMO impedance-based stability assessment 394
  generalized MIMO load interaction 391
  generalized MIMO source interactions 390

Power Electronic Converters: Dynamics and Control in Conventional and Renewable Energy Applications, First Edition. Teuvo Suntio, Tuomas Messo, and Joonas Puukko.
© 2018 Wiley-VCH Verlag GmbH & Co. KGaA. Published 2018 by Wiley-VCH Verlag GmbH & Co. KGaA.

control block diagram (*Continued*)
generalized SISO cascaded control 33
generalized SISO closed loop 178
generalized SISO impedance-based stability assessment 12
generalized SISO load interaction 38
generalized SISO source interactions 173
control delay, Padé approximation 108
control design
AC-current control 493
coupled-inductor superbuck 64, 474
DC-voltage control 493
DDR boost converter 213, 215, 321
DDR buck converter 174
discrete-inductor superbuck 331
PCM boost converter 258, 315, 325
PCM buck converter 178, 247
phase-locked loop 591
controller implementations
I controller 106, 108, 449, 451
P controller 106
PI controller 107, 226, 227, 271, 534
PID controller 105, 271, 295, 449
coupled inductor 19, 64, 65, 157, 160, 205, 219, 221, 330, 332, 475
cross-couplings 45, 549, 557–560, 622, 664, 665, 683
crossover frequency
gain margin 13, 325
phase margin 447, 457, 555, 556, 571, 576
RHP pole limitation 89
RHP zero limitation 325, 326
current-fed converter
boost converter 345
buck-boost converter 347
buck converter 342
current-fed inverter 515
non-inverting buck-boost converter 149
quadratic buck converter 348
sepic converter 347
superbuck converter 372
current-mode control
average-current-mode control 225
peak-current-mode control 190
self-oscillation control 125, 231

d

damping ratio, phase-locked loop 543
d-channel 550, 603, 644, 645
DC UPS, 36, 266, 278
DC-voltage control 493, 507, 514, 520, 533, 549, 563, 598, 606, 639, 640, 645, 646, 656, 669, 692–694
decoupling gains 497, 533, 549, 559, 561, 562, 633, 634, 644–646, 649, 664
differential power processing 468, 469
direct component 423
direct-duty-ratio 57, 125
control 8
direct-on-time control 125, 127
discontinuous conduction mode (DCM) 7, 57
distributed MPP tracking 465
dq-domain current control 622
duality transformation 6, 9, 20, 341, 342, 358, 377, 485
duty ratio 8, 27, 57, 62, 99, 101, 125, 128, 155, 163, 164, 174–176, 189, 190, 192–197, 199, 201–207, 209, 210, 213, 215, 218, 222, 223, 225, 226, 228, 231, 284, 351, 372, 379, 397, 404, 407, 411, 413, 415, 436, 441, 445, 446, 495, 551, 560, 612, 634, 635, 649, 651, 684, 690
gain 176, 189, 194, 196, 260, 406
dynamics 30, 32, 38, 48, 54, 92, 125, 212, 217, 267, 360, 364, 371, 408, 416, 437, 470, 499, 515, 518, 527, 536, 549, 550, 564, 592, 603, 637, 638, 640, 651, 652, 681, 687
capacitance 426, 470
modeling 7, 20, 45, 58, 66, 125, 189, 265, 355, 377, 403, 493, 681, 692
resistance 426, 429, 446, 470, 474, 518, 519, 523

e

equivalent circuit
  canonical equivalent circuit
    current-fed DC-DC converter 10, 43
    three-phase AC-DC converter 10
    three-phase DC-AC converter 10
  canonical equivalent circuit 8, 11
    voltage-fed DC-DC converter 9
  equivalent switching circuit (DC-AC) 508
  multiport network equivalent circuit (MISO)
    three-phase voltage-input-current-output converter (Y) 500
    three-phase voltage-input-voltage-output converter (G) 500
  multiport network equivalent circuit (SIMO) 87
  three-phase voltage-input-current-output converter (Y) 622
  three-phase voltage-input-voltage-output converter (G) 495
  two-port network equivalent circuit 28
    current-input-current-output converter 5
    voltage-input-current-output converter (Y) 189
    voltage-input-voltage-output converter (G) 268
error amplifier
  current-loop amplifier 225
  I-type 449
  PID-type 312, 447
  PI-type 226

f

feedback
  complementary sensitivity function 27
  loop gain 52, 84, 102, 300, 312, 321, 325
  robustness indices 95
  sensitivity function 93
fill factor 433
fixed-frequency operation 126, 128, 142, 163, 164
forbidden region 13, 14, 92–95
frequency response 4, 5, 16, 77, 86, 89, 105–108, 114–117, 226, 227, 249, 258, 259, 397, 450–452, 455–459, 471, 503, 505, 514, 523, 539, 542, 569, 589, 608, 653, 690, 692
  measurement 583, 598
full-order model 615, 633, 645, 648, 664
full-power processing 469

g

gain-bandwidth product 102
generalized modeling technique 126, 129
G parameter 5
grid-feeding operation 11, 18
grid-forming operation 18, 50
grid-parallel operation 17, 50, 53
grid-supporting operation 509
grid-voltage feedforward 533, 562, 587, 596, 599, 610, 611, 614, 616, 617, 619, 623, 624, 626, 628, 648, 651, 653, 655, 656, 674, 675

h

harmonic operation 196, 320

i

ideal input admittance 174, 237, 242, 305
ideal input impedance 101, 173, 174, 240, 361, 391, 393
ideal input-output transfer function 31, 33, 50
ideal output admittance 392
ideal output impedance 394
ideal output-input transfer function 643
impedance-based stability criterion 667
impedance shaping 678
input filter
  LC filter 95, 112, 349

input-voltage feedforward 174, 194
instability 14, 16, 179
interaction
  load interaction 19, 38, 54, 176, 239, 270, 390, 393
  source interaction 101, 173, 174, 244, 269, 390, 392
inverters 4, 15–18, 47, 50, 111, 351, 432, 435, 465
inverting buck-boost 137, 138
irradiance 424, 432, 434, 507
IV curve 426, 429–432, 434, 468

j

Jacobian matrix 60

k

K value 68, 87, 539

l

LC filter 95, 102, 111, 112, 181, 244, 246, 345, 349, 674
LCL filter 111, 113, 525, 528, 648, 653, 655, 656
L filter 550
linearized model, phase-locked-loop 536, 591
load effect 28, 189, 211, 250, 254, 255, 266, 273, 502, 503, 521, 558, 577, 620
load-transient response 181
loop gain
  controller 311
  design constraints 100
  gain-bandwidth product 102
loop shaping 310

m

MATLAB code 500, 501, 526, 528
maximum peak criteria (MPC) 94
maximum power point (MPP) 4, 395, 579
  tracking 432, 436, 437, 439, 444, 446, 451, 453
mode limit 190, 194, 196, 197, 199, 200, 204, 228, 291, 319
model verification
  inverter output admittance 645, 646, 656, 657, 668, 669
  inverter output impedance 16, 669, 671, 674
  open-loop dynamics 499, 510, 527, 681
modulator gain 31, 35, 97–99, 128, 129, 321, 325, 551, 587, 616

n

negative incremental resistance 185, 244, 361, 429, 482
negative sequence component 544, 545
non-inverting buck boost 139, 149, 151, 347, 368, 387
Nyquist plot 57, 87–90, 487
Nyquist stability criterion 13, 20, 41, 57, 87, 89, 95, 179, 271, 394, 482, 574, 668, 672

o

open-circuit input admittance 270
open-circuit input impedance 391, 408, 413
open-circuit output admittance 267, 268
open-circuit output impedance 177, 215, 217, 221, 241
open-circuit voltage 426, 430, 433, 434
open-loop control block diagram 503, 686
open-loop transfer function 31, 35, 97, 250, 500, 511, 521, 550, 587, 595, 605, 641, 650, 688, 691
output-current feedforward 177, 240, 241, 395
output filter
  LC filter 102
  LCL filter 111
  L filter 550
output impedance 254
output-voltage feedforward 394, 447

p

Padé approximation 108, 311, 543, 629
passive damping 524, 620, 665

peak current mode control
CCM modeling 244
comparator equation 290
DCM modeling 222
duty-ratio generation 224
harmonic operation mode 190
mode limit 190
peak voltage mode control 403
perturb and observe 432, 435
perturbation frequency
closed-loop converter 244
design 437
settling time 294
phase-locked loop (PLL) 15
photovoltaic (PV) cell
constant current region 521
constant power region 439
constant voltage region 521
current-voltage curve 517, 522
dynamic resistance 435
maximum power point (MPP) 521
open-circuit voltage 430
power-voltage curve 518, 576
short circuit current 433
photovoltaic (PV) generator
MPP tracking 436
power dynamics 461
stability 465
photovoltaic inverter 509, 523, 545, 567, 574, 598, 605, 625, 626, 628, 646, 656
PI controllers 106, 107, 226, 227, 278, 534, 538, 548, 590, 642, 691
polar plot 86, 87, 89
positive sequence component 535, 545
power invariance 68
pseudo-random binary sequence 249, 504

q

Q-channel 498, 501, 502, 560, 591, 609
quadrature component 11, 68
quality factor (Q) 113, 146, 149, 153

r

real-time simulator 542, 543, 575, 625, 627, 646, 656, 692
rectifier 11, 33, 37, 42, 44, 47, 69, 70, 494, 495, 500, 515, 533, 566, 681, 684, 686, 687, 689–691, 693, 694
reduced-order dynamics 633
remote sensing 277, 279, 304, 306, 307, 309, 310
resonant frequency 81, 102, 112, 113, 181, 304, 312, 321, 322, 326, 361, 368, 395, 447, 524, 553, 657
resonant peaking 110
RHP pole, control design constraint due to RHP pole 102
RHP zero, control design constraint due to RHP zero 102
Ridley model 249
RMS invariance 68
Routh array 85, 87, 88, 159
Routh Hurwitz 84–86, 218, 375

s

second-order system estimate
damping factor estimate 80, 541
feedback-loop crossover frequency 102
undamped natural frequency estimate 149, 541
settling time 96, 98, 99, 247, 294, 315, 321, 329, 444, 446, 450, 453–456, 459, 534, 541, 571, 692, 693
short-circuit current 426, 433, 434, 579
short-circuit input admittance 211, 215, 217, 221, 237, 241, 305
short-circuit input impedance 15, 242, 243, 246, 306
short-circuit output admittance 392, 408, 413
short-circuit output impedance 394
Simulink average model
DRR-controlled buck converter 254
PCM-controlled buck converter 253
PWM modulator 288
Simulink switched model
closed-loop converter 285
DDR-controlled buck converter 284
input filter 285
output filter 507, 525

Simulink switched model (*Continued*)
PCM-controlled buck converter 284
PWM modulator 284
single pole 79, 311
single zero 78, 298
small-signal modeling
average mode 57
linearization, Jacobian matrix 60
buck converter example 61
conduction mode 57
coupled-inductor modeling 66
three-phase rectifier example 69
solar cell 423–427, 429
source effect
source-affected transfer functions of PV inverter 474
stability
conditional stability 27
generalized Nyquist stability criterion 87
instability 305
Nyquist criterion 394
robustness indices 95
Routh array 87
Routh Hurwitz 86
unconditional stability 27
state space 7–9, 59, 60, 63, 65, 73, 74, 76, 126, 130, 132–135, 138–140, 142–145, 147–149, 151, 152, 154, 157, 158, 160, 164, 165, 167, 168, 170, 171, 189, 193, 201, 209, 211–217, 219, 220, 222–224, 232, 234, 235, 279, 287, 288, 355, 360, 361, 363, 367, 370, 374, 378, 380, 384, 385, 388, 406, 411, 415, 418, 419
averaging technique 57, 125
step response
AC current control 493, 559, 606
DC voltage control 493, 520
phase-locked loop 591, 609
synchronous reference frame
amplitude invariance 68
power invariance 9, 42
RMS invariance 68

t

transfer function
control-to-input transfer function 375, 472, 479, 480, 690
control-to-output transfer function 52, 83, 155, 211, 221, 273, 413, 472, 478–480, 518
input admittance 145, 148, 152, 167
input impedance 643
input-to-output transfer function 637, 643
output admittance 392, 637
output-to-input transfer function 643
second-order transfer function 80
single pole 79
single zero 298
transient performance
indices 27, 96
load-transient response 95
settling time 329

u

unbalanced grid voltages 543, 544, 577
underdamped natural frequency
phase-locked loop 80

v

variable frequency control 7, 189
voltage-fed inverter 111, 493–496, 498, 500, 502–506, 508, 516, 533, 548–553, 560, 563, 567, 587, 588, 591, 595, 596, 602, 610
voltage-mode control 125, 231

y

Y-parameters 29, 44, 249, 500

z

Z-parameters 5, 29, 44, 355, 357